

Linear Circuit Theory

L01: Property of Electrical Elements and voltage current relation

- Basic property of electrical Elements
- Voltage current relation in electrical elements
- Basic numerical Example


Basic property of electrical Element


(Resistance (R), Inductance (L), Capacitance(C))


- **Linear and non linear:** Proportionality ratio between input and output remain constant


$$y(t) = f(x(t)), \quad \frac{y(t)}{x(t)} = k$$

(a) $y(t) = 2x(t)$ (b) $y(t) = 2x(t) + 3$ (c) $y(t) = 2x^2(t)$

• Resistance (R, ) $\rightarrow V(t)=R I(t)$

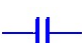• Capacitor (C, ) $\rightarrow Q(t)=CV(t)$

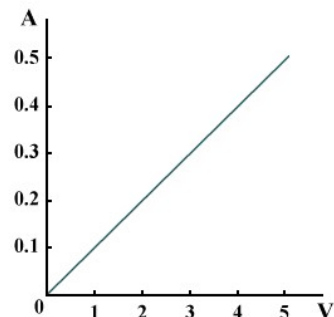• Inductor (L, ) $\rightarrow \phi(t) = L I(t)$




*Equation $V(t)= 2I(t) + 3$ is a linear relationship or not ???

➤ Unilateral and Bilateral Elements:

characteristics of an element does not change after changing the polarity of energy source

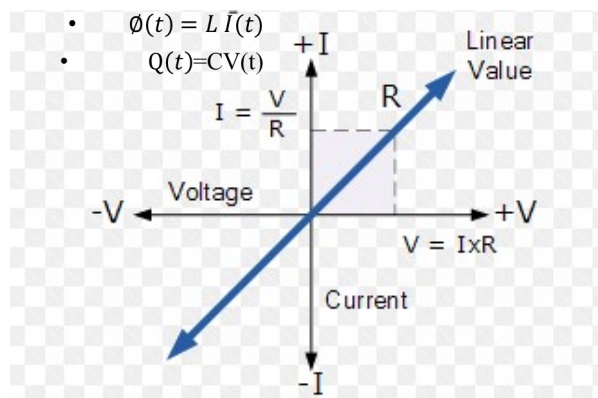- Electrical Elements (R,L,C) are bilateral Elements
- Electronics elements (diode ,transistor etc.) are Unilateral elements




➤ **Active and Passive Components:**

Response (Output) across the elements can't be greater than excitation

- Electrical Elements (R,L,C) are Passive Elements
- Electronics elements (diode ,transistor etc.) are Active elements

Voltage and current relation in R,L , C

Resistance

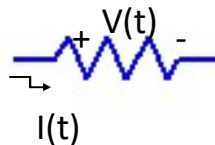

$$V(t) = RI(t)$$

$$I(t) = \frac{V(t)}{R}$$

➤ Same behavior for both AC and DC Supply

Capacitor

$Q(t) = C v(t)$
 $I(t) = C \frac{dv(t)}{dt}$
 $v(t) = \frac{1}{C} \int I(t) dt$

For DC Supply:

In SC condition
 $\frac{dv(t)}{dt} \rightarrow$ very high
 $I(t) \rightarrow$ very high

In SS condition
 $\frac{dv(t)}{dt} = 0$ $I(t) = 0$

Capacitor voltage does not change instantaneously $v_c(0^-) = v_c(0^+)$

Equivalent model

For AC


$v_c(t) = \frac{1}{C} \int I(t) dt$
 $v_c(t) = \frac{1}{C} \frac{I(\omega)}{\omega} \pm \frac{v_c(0)}{\omega}$
 $v_c(t) = \frac{1}{C} \frac{I(\omega)}{\omega} \quad [v_c(0) = 0]$
 $v_c(t) = \frac{1}{|\omega C|} \cdot I(t - 90^\circ)$ (voltage lag by current 90°)

Q. Calculate $I(0)$, $v_c(0)$, $I(\alpha)$, $v_c(\alpha)$


$v_L(t) = |NL| I(t \mp 90^\circ)$, $v_L(t)$ leads $I(t)$ by 90°

Inductor current does not change Instantaneously ~~+~~
 $I_L(0^-) = I_L(0^+)$


Equivalent model

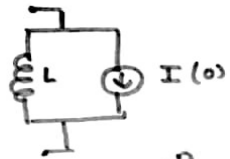

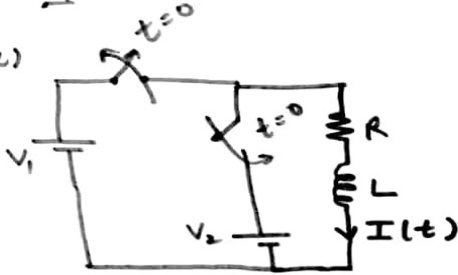Prob.: $I(0)$, $I(\infty)$, $v_L(0)$, $v_L(\infty)$



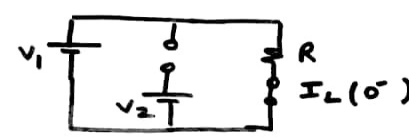
$t < 0$ $I_L(0^-) = \frac{V_1}{R} = I_L(0)$



$t = 0$

$$-V_2 + R \left(\frac{V_1}{R} \right) + v_L(0) = 0$$


$v_L(0) = V_2 - V_1$

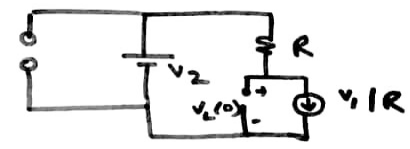

$t = \infty$

$I_L(\infty) = \frac{V_2}{R}$


$v_L(\infty) = 0$

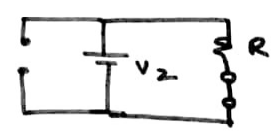

Conceptual Question:

1. Which one have more resistance 1KW Heater or 2KW and why

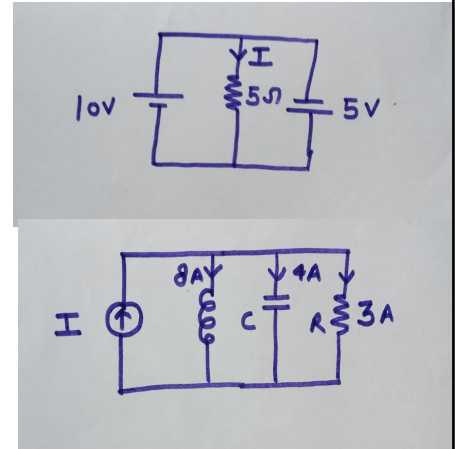2. Calculate the current in both the figure as shown



In Coming Lecture

- Answer of previous seat question
- Complete study of nodal analysis
- concepts of super node
- Concepts of dependents source
- Numerical Example

Thank you

