

Linear Circuit Theory


L03: Concepts of dependent source

- Solution of Question of last lecture
- Concepts of dependent source
- Questions based on nodal analysis

**Calculate value of
(a) V_A , V_B , V_C ??**

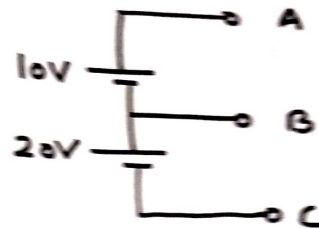
(b) V_{AB} , V_{BC} , V_{CA}

- $V_{AB} = V_A - V_B = 10V$,
- $V_{BC} = V_B - V_C = 20V$,
- $V_{CA} = V_C - V_A = -30$



(a)

(b) Calculate Current


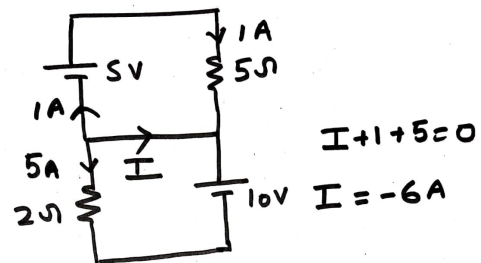


(C) Calculate V_0

$$\left(\frac{V_0}{2} - 5\right) \times 1 + \left(2 + \frac{V_0}{2}\right) \times 1 + V_0 - \left(1 - \frac{V_0}{2}\right) = 0$$


$$V_0 = \frac{8}{5} \text{ V}$$

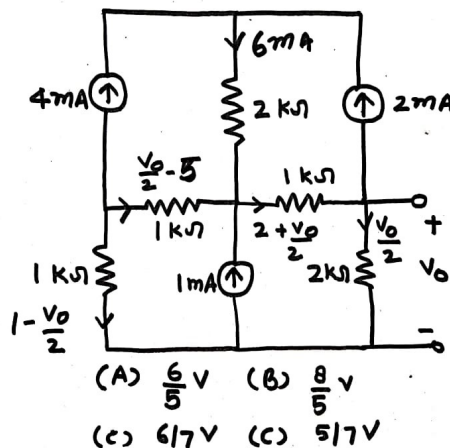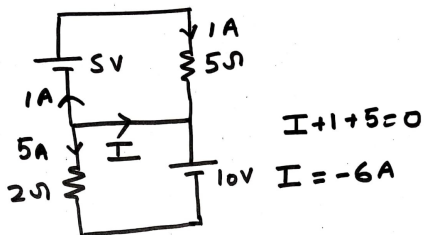(d) Calculate Voltage across current source




What is independent and what is dependent ?

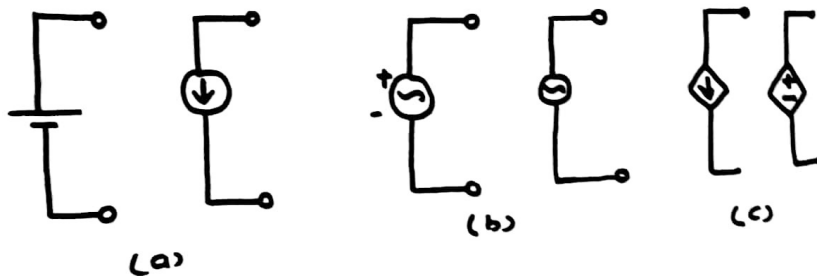When the magnitude of a voltage or current source depends upon another parameter of the circuit




- (a) Independent DC voltage and current source
- (b) Independent AC voltage and current source
- (b) dependent DC voltage and current source

Concept behind the dependent source

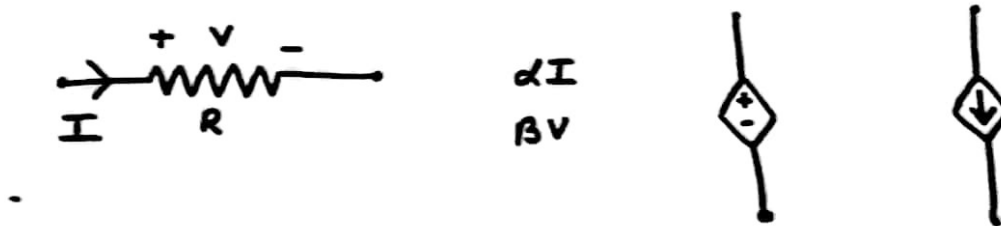

- Symbol- Type of source
- Magnitude- dependent quantity

Types of dependent source

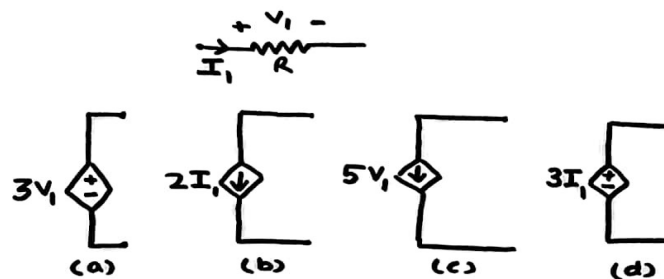

(a)VDVS (b)CDCS (c)VDCS (d)CDCVS

*In case of dependent source same rule is applied as on independent source for solving a circuit problem

Example problem

Find I_1 & V_1

NODE - A, B, C, D

VOLTAGE - V_A, V_B, V_C

D & C make supernode
 $V_C = -5V$


UNKNOWN V_A, V_B, I_1, V_1

① NODE A


$$\frac{V_A - 6}{2 + 4} + 3 + \frac{V_A - V_B - 3V_1}{4 + 2} = 0$$

② NODE-B $\frac{V_B - V_A + 3V_1}{2 + 4} + \frac{V_B - V_C}{4} = 4I_1 = 0$
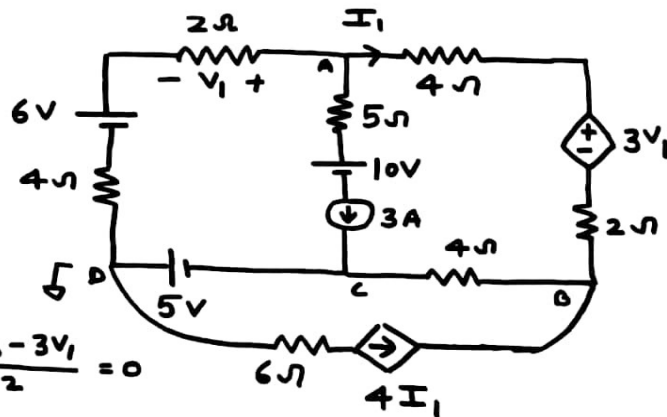
$$V_1 = 2 \left(\frac{V_A - 6}{4 + 2} \right), \quad I_1 = \frac{V_A - 3V_1 - V_B}{4 + 2}$$




Tutorial Sheet:

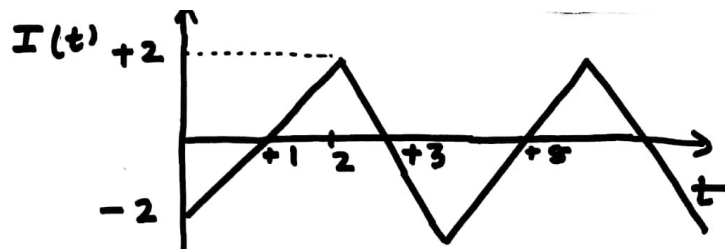


(a) If $I(t)$ current across 2mH inductor calculate voltage $V(t)$

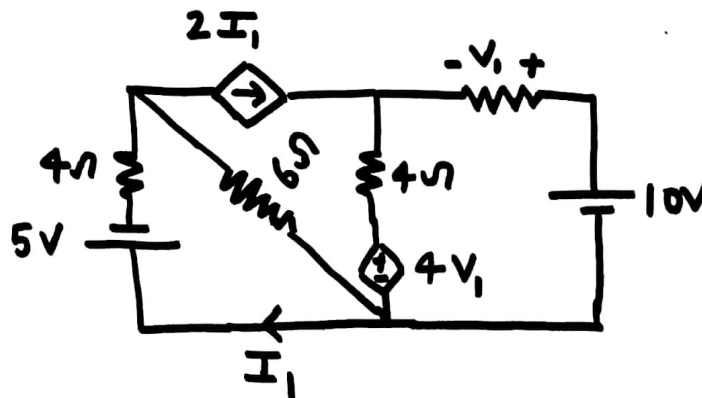(b) Calculate V_1 and I_1 as shown in figure



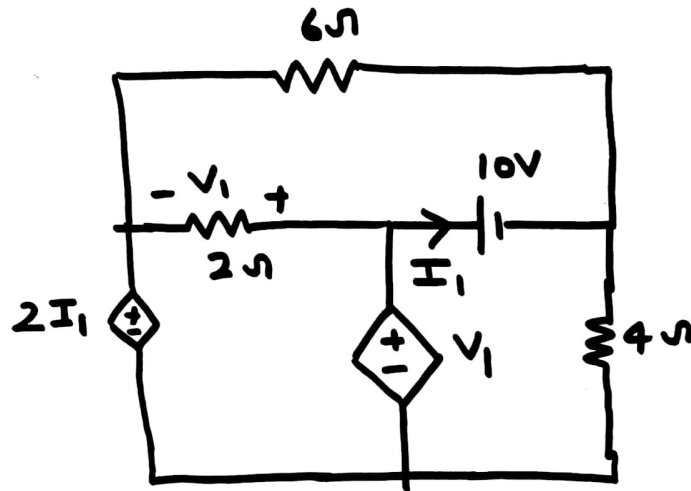(c) Calculate V_1 and current in 4 ohm resistance



In Next Lecture

- Answer of tutorial seat Problem
- Concepts of super mesh analysis
- A seat of numerical examples

Thank you

