

# Linear Circuit Theory

L04: Concepts of Mesh and Super mesh analysis

- Solution of last lecture question
- Concepts of mesh and super mesh
- Questions based on mesh analysis

T  
u  
t  
o  
r  
i  
a  
l  
S  
h  
e  
e  
t

Qm-1  $L = 2 \text{ mH}$ ,  $v_L(t) = ?$


$$I(t) = \begin{cases} 2t - 2 & 0 < t < 2 \\ -2t + 6 & 2 < t < 4 \end{cases}$$

$$\frac{dI(t)}{dt} = \begin{cases} 2 & 0 < t < 2 \\ -2 & 2 < t < 4 \end{cases}$$

$$v_L(t) = L \frac{dI(t)}{dt} = \begin{cases} 4 \text{ mV} & 0 < t < 2 \\ -4 \text{ mV} & 2 < t < 4 \end{cases}$$

Fig-1


Q-2 Calculate  $V_1$  and  $I_1$

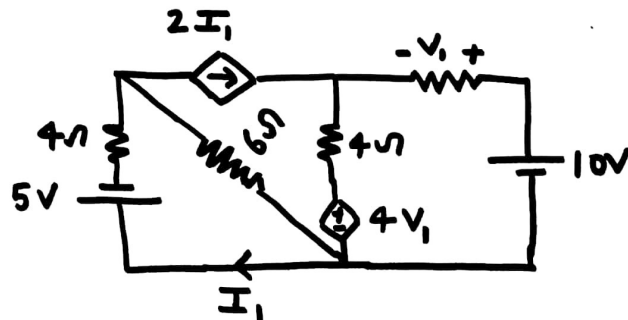

$$-V_1 + 10 - 4V_1 + 4\left(\frac{V_1}{2} + 2I_1\right) = 0$$

$$-6I_1 + 5 + 4I_1 = 0$$

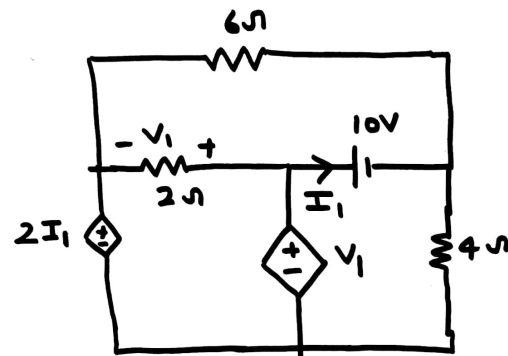(c) Calculate  $V_1$  and current in 4 ohm resistance



$$V_1 - 2I_1 = V_1$$




$$I_1 = 0$$

$$\frac{0 - (V_1 - 10)}{6} + \frac{V_1 - 10}{4} = 0$$

$$V_1 = 10$$
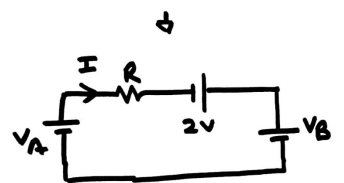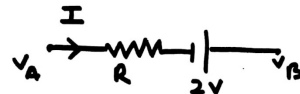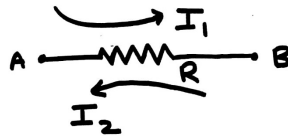
### Concepts of Mesh analysis:

- Selection of mesh
- Assumption of mesh current
- Apply the KVL



$$-V_A + IR - 2 + V_B = 0$$

$$I = \frac{V_A - V_B + 2}{R}$$

### KVL in a loop

KVL in ABCDA


$$R_2(I_1 + I_2) + V_1 +$$

$$R_3(I_1 + I_3) + V_5$$


$$-V_2 + R_4(I_1 - I_4)$$

$$+ V_3 + R_1(I_1 - I_5)$$

$$= 0$$

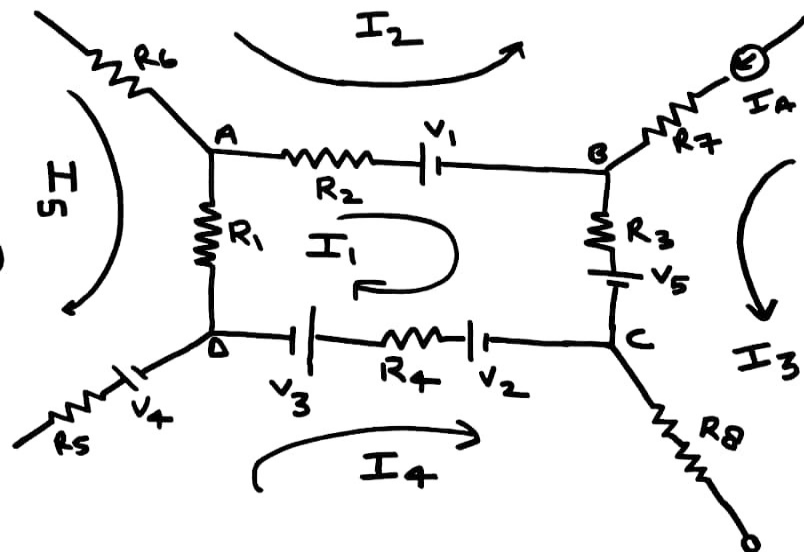


Solve the problem

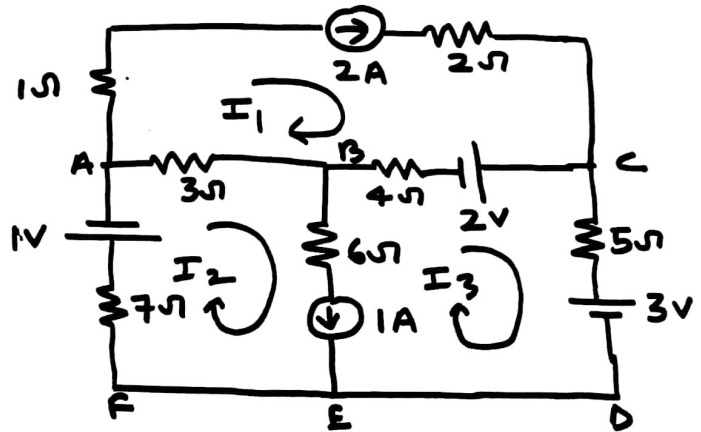




$$\begin{aligned}
 I_1 &= 2 \\
 I_2 - I_3 &= 1 \\
 3(I_2 - I_1) + 4(I_3 - I_1) - 2 + \\
 5I_3 + 3 + 7I_2 + 1 &= 0
 \end{aligned}$$

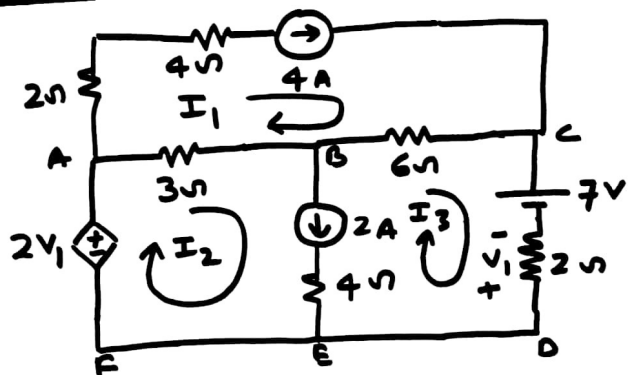Super mesh problem  
with dependent source



$$\begin{aligned}
 I_1 &= 4 \\
 I_2 - I_3 &= 2 \\
 3(I_2 - I_1) + 6(I_3 - I_1) \\
 + 7 + 2I_3 - 2V_1 &= 0 \\
 V_1 &= -2I_3
 \end{aligned}$$

Tutorial problem

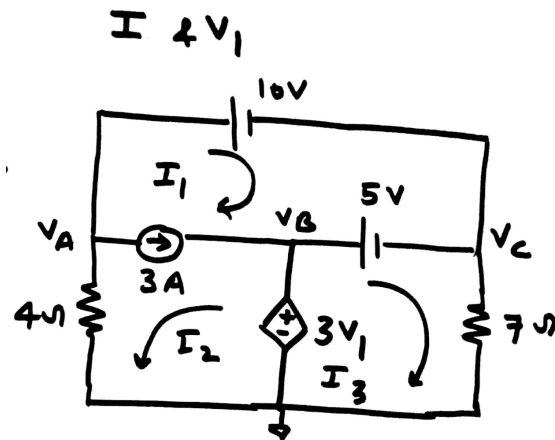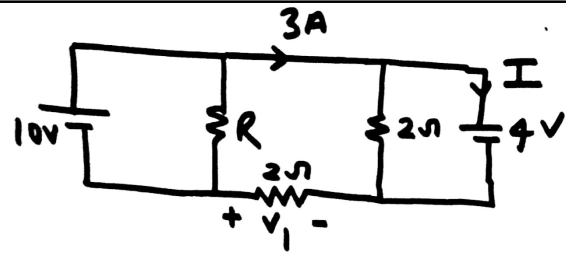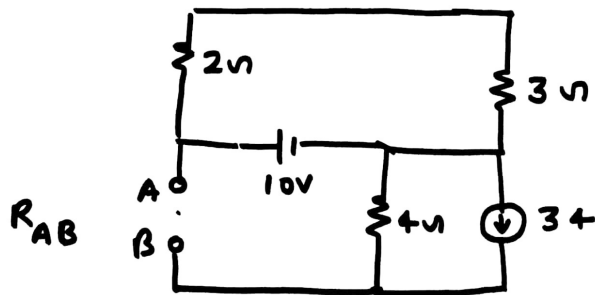

Next lecture

- Discussion on these problem
- Concept of mutual Inductance
- Problem and solution based on mutual inductance

Thank you